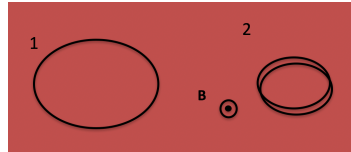


Loop 1 sits in a uniform field B which is increasing in magnitude. Loop 2 has the SAME LENGTH OF WIRE looped (coiled) to make two (smaller) loops. How do the





induced EMFs compare?

- A. $EMF(1) = 4 EMF(2)$
- B. $EMF(1) = 2 EMF(2)$
- C. They are both the same.
- D. $EMF(2) = 4 EMF(1)$
- E. $EMF(2) = 2 EMF(1)$


The switch is closed at $t = 0$. Which graph best shows $I(t)$?

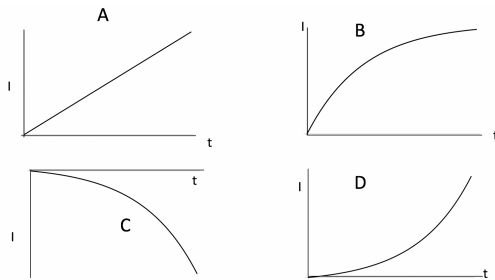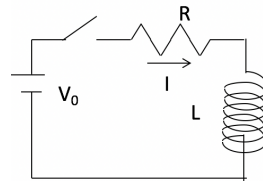E) None of these (they all have a serious error!)




The switch is closed at $t = 0$. What can you say about $I(t = 0+)$?

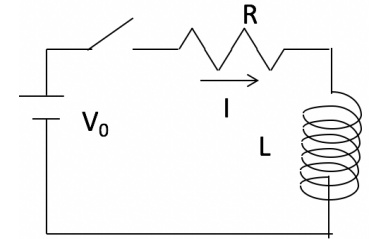- A. Zero
- B. V_0/R
- C. V_0/L
- D. Something else!
- E. ???



The switch is closed at $t = 0$. What can you say about the magnitude of ΔV (across the inductor) at $(t = 0+)$?

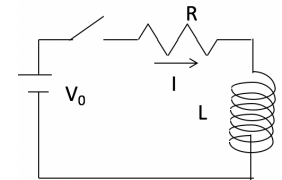- A. Zero
- B. V_0
- C. L
- D. Something else!
- E. ???



The complex exponential: $e^{i\omega t}$ is useful in calculating properties of many time-dependent equations. According to Euler, we can also write this function as:

- A. $\cos(i\omega t) + \sin(i\omega t)$
- B. $\sin(\omega t) + i \cos(\omega t)$
- C. $\cos(\omega t) + i \sin(\omega t)$
- D. MORE than one of these is correct
- E. None of these is correct!

What is $|2 + i|$?

- A. 1
- B. $\sqrt{3}$
- C. 5
- D. $\sqrt{5}$
- E. Something else!